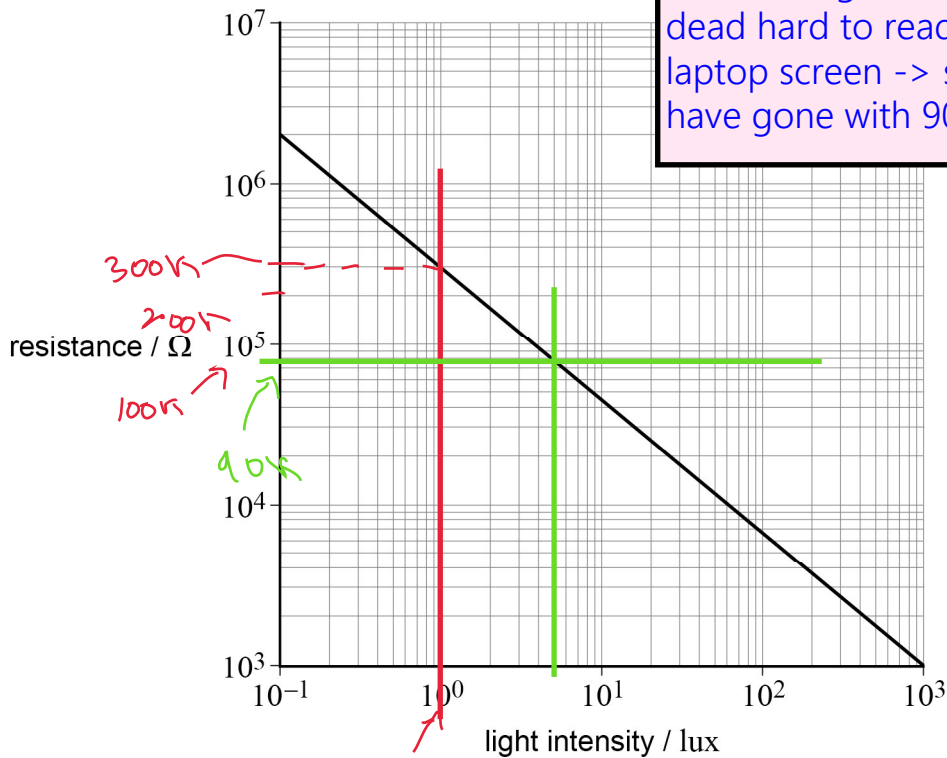


0 6


Figure 11 shows how the resistance of an LDR varies with light intensity.

Figure 11



The LDR is used as part of an alarm system in a dim room. Figure 12 shows one proposal for a sensor circuit for this system.

Figure 12

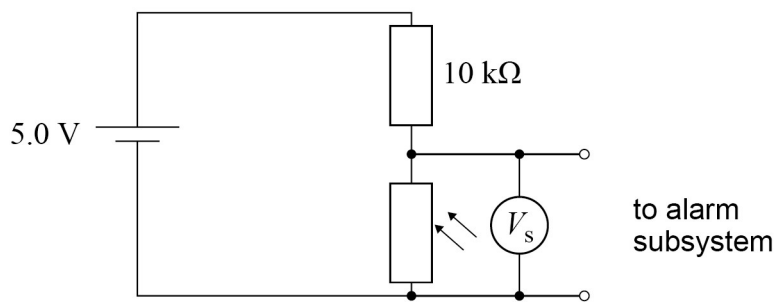

The power supply to the sensor has an emf of 5.0 V and a negligible internal resistance. A negligible current is drawn from the sensor circuit by the alarm subsystem.

A light beam illuminates the LDR. When the light beam is broken the LDR is not illuminated by the light beam. This causes the alarm to sound.



Table 3 shows how the light intensity at the LDR changes.


Table 3

	Light intensity / lux
LDR illuminated by light beam	4.0
LDR not illuminated by light beam	1.0

R
90kΩ ✓
300kΩ

- 0 6 . 1** Show that the current in the sensor circuit when the LDR is **not** illuminated by the light beam is approximately $16 \mu\text{A}$.

[2 marks]

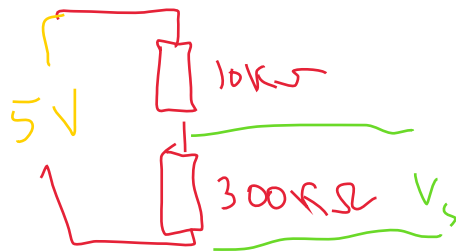

$$\frac{V}{R} = I$$

$$\frac{5}{310 \times 10^3} = 1.6 \times 10^{-5} = 16 \mu\text{A}$$

- 0 6 . 2** The alarm sounds when the potential difference V_s across the LDR changes by more than 25% of the power supply emf.

Discuss whether the circuit shown in **Figure 12** is suitable.
Support your answer with a calculation.

[3 marks]

$$V_s \text{ dark} = \frac{300}{310} \times 5$$

$$4.8 \text{ V}$$

$$V_s \text{ light} = \frac{90}{90+10} \times 5$$

$$4.5 \text{ V}$$

$$\Delta V = 0.3 \text{ V} \quad \text{this is less than}$$



$$25\% \text{ of emf} \quad (25\% \text{ of } 5 \text{ V} = 1.25 \text{ V})$$

END OF SECTION A

Turn over ►



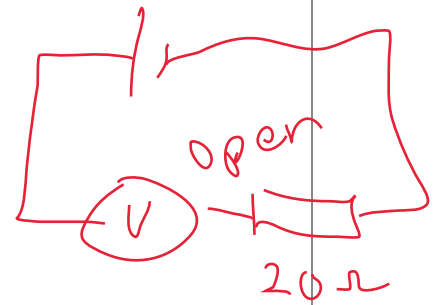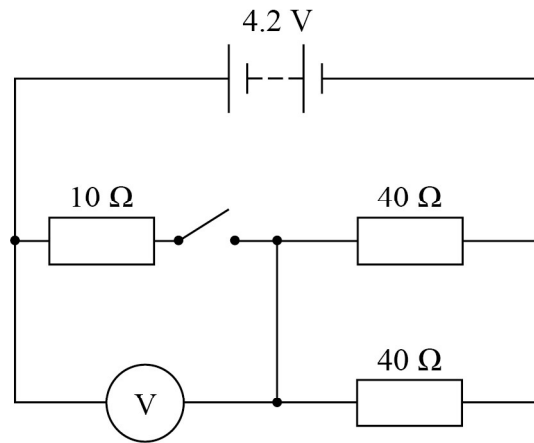2 7 The battery in this circuit has an emf of 4.2 V and negligible internal resistance.




What are the readings on the voltmeter when the switch is open (off) and when the switch is closed (on)?

[1 mark]

	Open	Closed	
A	0 V	2.1 V	<input type="radio"/>
B	4.2 V	2.1 V	<input type="radio"/>
C	0 V	1.4 V	<input type="radio"/>
D	4.2 V	1.4 V	<input checked="" type="radio"/>

Open is 4.2V because the voltmeter has an extremely high resistance and is connected in series with a 40s in parallel - it therefore takes all the voltage.

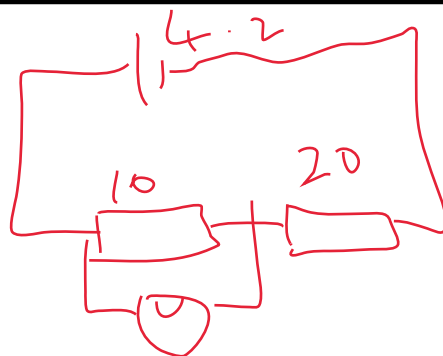Closed. The two 40s are in parallel making a 20ohm. This twenty is in series with a 10ohm. Voltmeter is over the 10 so now we have a potential divider:




$$V_v = 4.2 \times \frac{10}{10 + 20} = 1.4 \text{ V}$$

Turn over ►



2 8

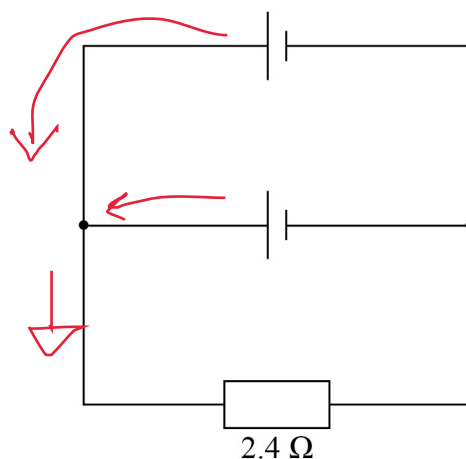Two identical batteries each of emf 1.5 V and internal resistance 1.6 Ω are connected in parallel. A 2.4 Ω resistor is connected in parallel with this combination.



$$E = 1.5$$

each

$$r = 0.8 \Omega$$

(two 1.6 in
parallel)


What is the current in the 2.4 Ω resistor?

A 0.38 A

B 0.47 A

C 0.75 A

D 0.94 A

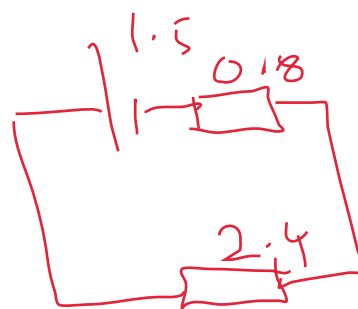

[1 mark]


$$\frac{V}{R} = I \Rightarrow I = \frac{1.5}{0.8 + 2.4}$$

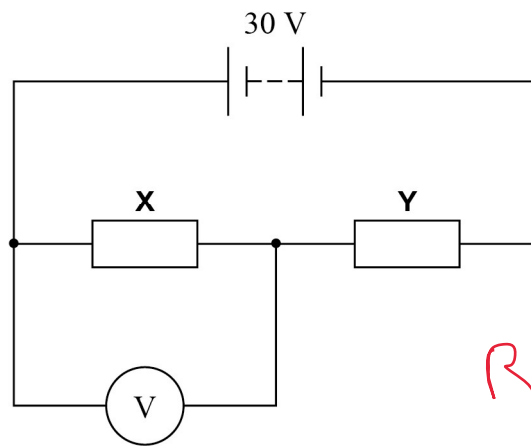0.47 A



2 9

Two resistors **X** and **Y** are connected in series with a power supply of emf 30 V and negligible internal resistance. The resistors are made from wire of the same material. The wires have the same length. **X** uses wire of diameter d and **Y** uses wire of diameter $2d$.



$$R = \frac{\rho L}{A}$$

$$R = \frac{\rho L}{\pi r^2}$$

$$R \propto \frac{1}{r^2}$$

What is the reading on the voltmeter?

[1 mark]

- A 10 V
- B 15 V
- C 20 V
- D 24 V**

radius y is twice radius x
 A_y is $4A_x$
 So R_y is $R_x/4$
 ie resistance of Y is 1/4 times resistance of x.
 $R_x = 4R_y$

$$V_o = V_{in} \frac{R_x}{R_x + R_y}$$

Turn over

Sub in $4R_y$ for R_x

$$V_o = V_{in} \frac{4R_y}{4R_y + R_y} \Rightarrow V_o = V_{in} \frac{4R_y}{5R_y}$$

$$\therefore V_o = \frac{30 \times 4}{5} = 24V$$

Turn over ►

