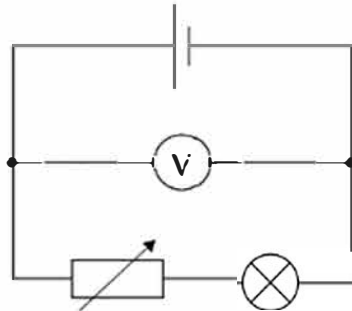


0 7

Figure 9 shows a practical circuit in which a variable resistor is used to control the brightness of a lamp. The voltmeter reading is monitored as the variable resistor is adjusted to make the lamp brighter.

Figure 9



0 7 . 1

Explain why the reading on the voltmeter decreases as the brightness of the lamp increases.

[2 marks]


As the brightness of the bulb increases the current in the circuit increases. This means that the I through the internal resistance also increases and then from $V=IR$ this means that the lost voltage across r must also increase. Therefore the terminal pd as measured by the voltmeter decreases

0 7 . 2

The variable resistor is adjusted so that the lamp is at its brightest. The reading V_1 on the voltmeter is noted. A second identical cell is then connected in parallel with the cell in Figure 9. The new reading V_2 on the voltmeter is noted.

Explain why V_2 is greater than V_1 .

[2 marks]

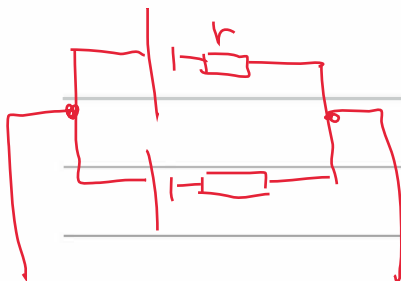

Terminal pd is increasing - this is because we have two internal resistors connected in parallel so their combined resistance decreases meaning that the value of the lost voltage $v=Ir$ also decreases.

4

Turn over ►




2 1 A rubber belt in an electrostatic machine has a width of 0.1 m and moves with speed 0.4 m s^{-1} . Each square metre of the belt carries a charge Q coulomb. The charge is removed and transferred to a metal sphere.

Area of belt
moving up in 1 sec
 $= 0.4 \times 0.1 =$
 0.04 m^2

o
o o

Charge is $0.04Q$

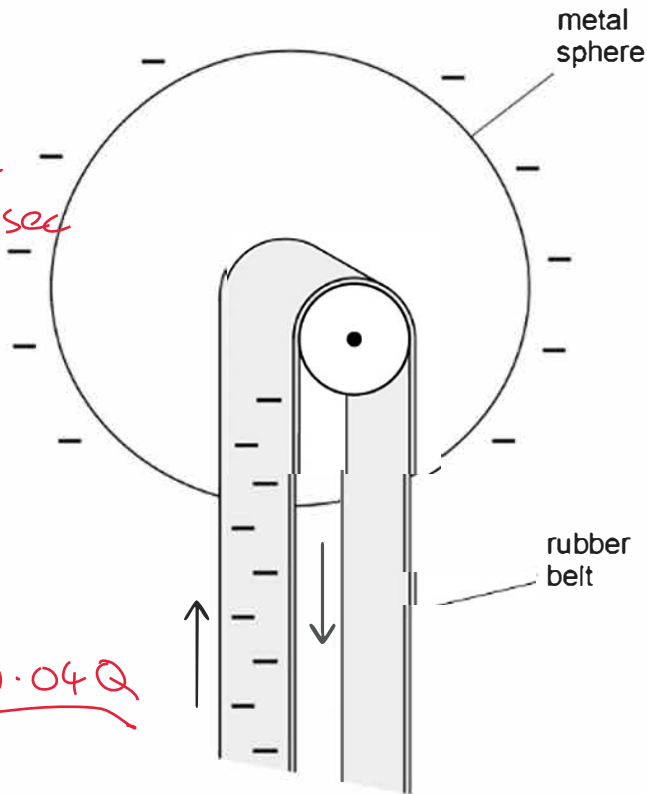

What is the charge collected by the sphere each second?

[1 mark]

- A $0.016Q$
- B $0.04Q$**
- C $0.25Q$
- D $4Q$



2 2

Charged plates **X** and **Y** have a potential difference 1.5 V between them.



Which particle gains 3.0 eV of kinetic energy when moving from **Y** to **X**?

[1 mark]

A proton

B positron

C electron

D alpha particle

1eV is the energy gained by 1e of charge as it accel through 1v. We have 1.5V so each e of charge gains 1.5eV. Since there are 3eV this must mean we have a particle with a double charge


Turn over ►



2 5

Two cylindrical wires **P** and **Q** are of equal length and made of the same material. The diameter of **P** is greater than that of **Q**.

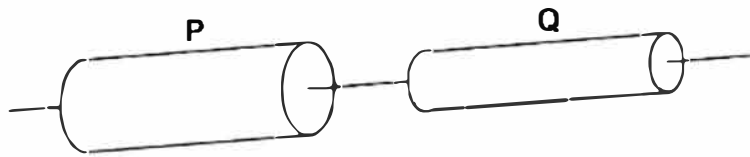P and **Q** are connected in series and the ends of this arrangement are connected to a power supply.



Which two quantities are the same for **P** and **Q**?

[1 mark]

A	potential difference across wire	resistivity	<input type="checkbox"/>
B	resistivity ✓	current ✓	<input checked="" type="checkbox"/>
C	current	resistance	<input type="checkbox"/>
D	resistance	potential difference across wire	<input type="checkbox"/>


Turn over for the next question

same material therefore same resistivity
connected in parallel so same I

Turn over ►



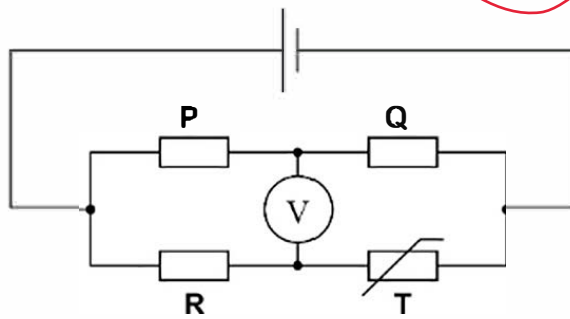2 6 In the circuit below, the initial voltmeter reading is zero.



so $\frac{P}{Q} = \frac{R}{T}$
 $T \downarrow \Rightarrow \frac{R}{T} \uparrow$
 and $V \uparrow$

The temperature of the negative temperature coefficient thermistor **T** is then increased.

Which change to the circuit could restore the voltmeter reading to zero?

[1 mark]

- A Decreasing the resistance of **R**. *- 'o' will $\downarrow R/T$ ✓✓✓*
- B Increasing the resistance of **R**. *will increase $V \times$*
- C Decreasing the resistance of **P**. *$P/Q \downarrow \times$*
- D Increasing the resistance of **Q**. *$\frac{Q}{T} \uparrow \times$*

2 7 An electric motor lifts a load of weight **W** through a vertical height **h** in time **t**. The potential difference across the motor is **V** and the current through it is **I**.

What is the efficiency of the motor?

[1 mark]

- A $\frac{Wh}{VI}$ *Power Out = $\frac{E}{t} = \frac{W \times h}{t}$*
- B $\frac{VI}{Wh}$ *Power In = VI*
- C $\frac{Wh}{VI}$ *effe: $\frac{(\frac{W \times h}{t})}{VI} \Rightarrow \frac{Wh}{tVI}$*
- D $\frac{VI}{Wh}$

