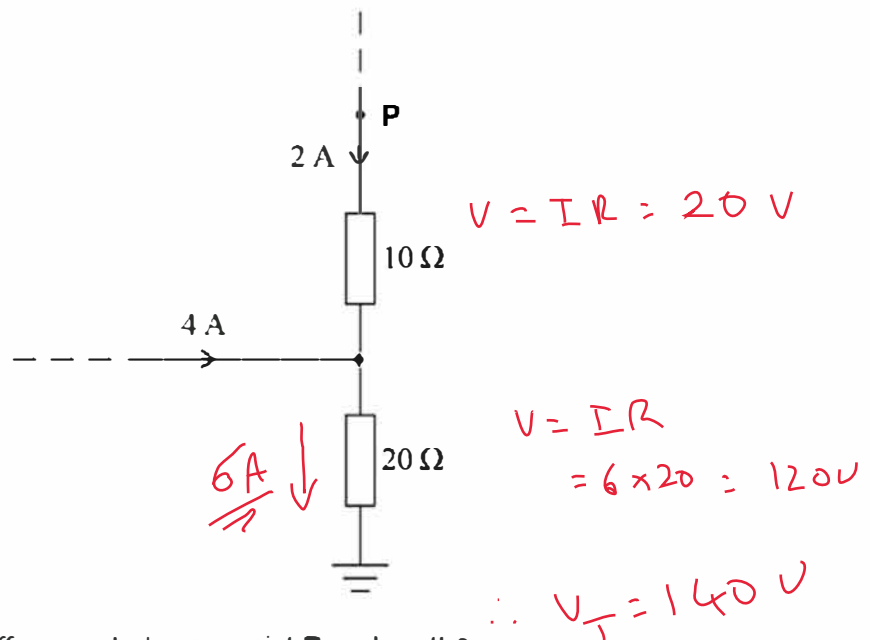


2 3

The diagram shows part of a circuit and the currents in the circuit.



What is the potential difference between point P and earth?

[1 mark]

A 60 V

B 100 V

C 120 V

D 140 V

2 4

A voltmeter has a resistance of 4.0 kΩ and reads 1.0 V for every scale division on the meter.

A power supply of emf 20 V and negligible internal resistance is connected across this voltmeter and a resistor in series. The voltmeter reads two divisions.

What is the value of the resistor?

[1 mark]


A 44 kΩ

B 36 kΩ

C 4.4 kΩ


D 3.6 kΩ

$V = IR$

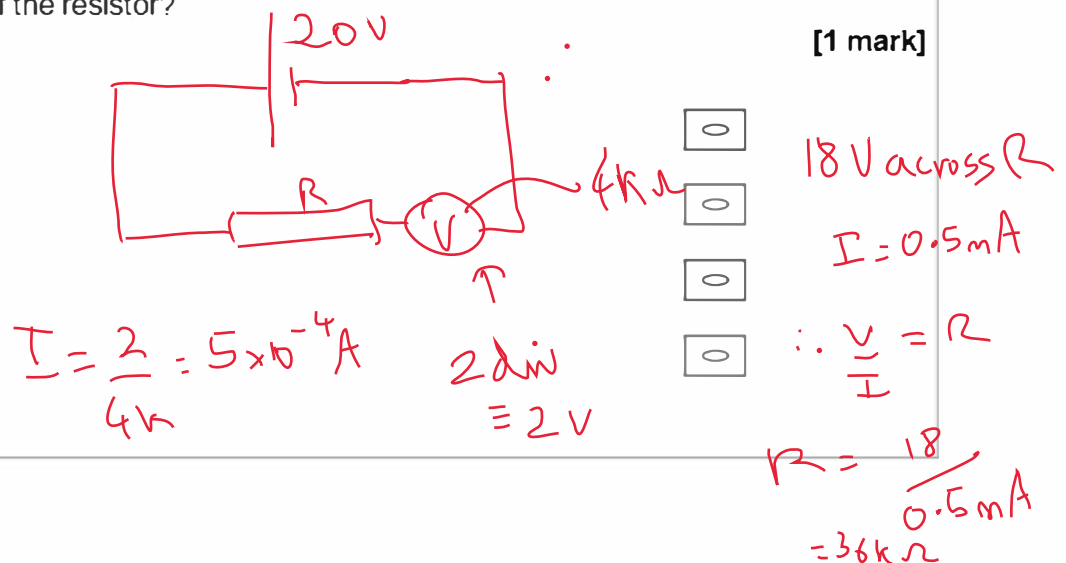


2 8

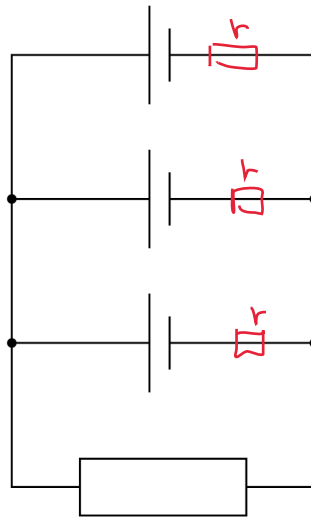A resistor of resistance  $R$  and three identical cells of emf  $E$  and internal resistance  $r$  are connected as shown.



Total  $r = \frac{r}{3}$

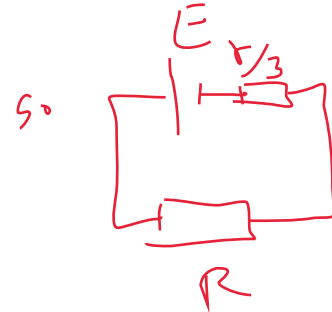

What is the current in the resistor?

$I = \frac{V}{R} = \frac{E}{\frac{r}{3} + R}$

[1 mark]

**A**  $\frac{3E}{(3R+r)}$

**B**  $\frac{9E}{(3R+r)}$

**C**  $\frac{E}{R}$

**D**  $\frac{3E}{R}$

Algebra.

$\frac{E}{\frac{r}{3} + R} = \frac{3E}{r + 3R}$

(Don't believe me - make up values for  $E$ ,  $r$  &  $R$  & check)


Turn over for the next question

Turn over ►



**2 9** In the circuit, the reading of the voltmeter is  $V$ .

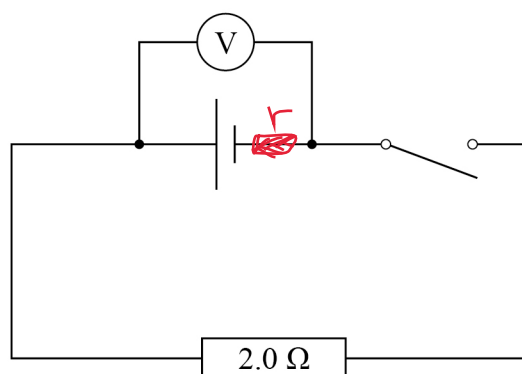When the switch is closed the reading becomes  $\frac{V}{3}$ .



- So  $\frac{2V}{3}$  dropped  
over  $r \rightarrow$   
ie twice that  
over  $2.0\Omega$  so  
must be  $4\Omega$ .

What is the internal resistance of the cell?

[1 mark]

A  $0.33\ \Omega$

B  $0.67\ \Omega$

**C**  $4.0\ \Omega$

D  $6.0\ \Omega$

END OF QUESTIONS

